

**QUESTION 4** (continued)

c) Draw a digital circuit for the keypad controller.

You may use any gates, flip flops, or components described in class.

